

HDL Week 2

Jochem Arends (485637)

Self Test Chapter 3

```
architecture arch of gate_network is
begin
-- concurrent assignment statements operate in parallel
-- d(1) selects bit 1 of standard logic vector D
    x <= a and not(b or c) and (d(1) xor d(2));
-- sroccess must declare a sensitivity list
-- sensitivity list includes all signals which can change the outputs
    process (a, b, c, d)
    begin
        -- statements inside a process execute in sequential order
        y <= a and not(b OR c) and (d(1) xor d(2));
    end process;
end arch;
```

1. *Is this a structural, behavioral, or RTL description?*

This is a RTL description cause the circuit is described in the relationship between signals.

2. *What is the purpose of a generic?*

The purpose of generics is to create flexible components.


3. *What is the purpose of a configuration statement?*

TODO

4. *In our tutorial there is an adder, is this a structural, behavioral, or RTL description?*

The adder from the tutorial uses a RTL description because the behaviour is described in terms of relationships between signals.

 5. *Draw the schematics of a full adder and make a structural VHDL description*



Exercises Chapter 3

1. *Simulate in Quartus the behavioral VHDL of a 3-bit adder.*

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity adder is
port (
    a, b: in std_logic_vector(2 downto 0);
    sum: out std_logic_vector(2 downto 0);
    carry: out std_logic
);
end adder;

architecture arch of adder is
begin
    process (a, b)
        -- intermediate carry
        variable int_carry: std_logic;
    begin
        -- reset carry
        int_carry := '0';

        for i in 0 to a'length-1 loop
            -- set sum bit
            if (a(i) = '0' and b(i) = '0' and int_carry = '1')
            or (a(i) = '0' and b(i) = '1' and int_carry = '0')
            or (a(i) = '1' and b(i) = '0' and int_carry = '0')
            or (a(i) = '1' and b(i) = '1' and int_carry = '1') then
                sum(i) <= '1';
            else
                sum(i) <= '0';
            end if;

            -- determine carry out
            if (a(i) = '0' and b(i) = '1' and int_carry = '1')
            or (a(i) = '1' and b(i) = '1' and int_carry = '0')
            or (a(i) = '1' and b(i) = '0' and int_carry = '1')
            or (a(i) = '1' and b(i) = '1' and int_carry = '1') then
                int_carry := '1';
            else
                int_carry := '0';
            end if;
        end loop;

        -- set final carry out
        carry <= int_carry;
    end process;
end arch;

```

1. Implement the 3-bit adder on the MAX 10 board.

I have no access to such board at the moment.

2. *Simulate in Quartus a structural description of a half adder.*

I have pasted an image of the simulation at the end of this document.

Self Test Chapter 4

```
architecture arch of gate_network is
begin
    x <= a and not(b or c) and (d(1) xor d(2));
    y <= (d(1) xor d(2));
end
```

1. *Which value, x or y is first evaluated?*

They are executed simultaneously since signal assignment is concurrent.

2. *Give the behavioral description of a 2 to 4 decoder.*

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity decoder is
port (
    a: in std_logic_vector(1 downto 0);
    d: out std_logic_vector(3 downto 0)
);
end decoder;

architecture arch of decoder is
begin
    process (a)
    begin
        case a is
            when "00" => d <= "0001";
            when "01" => d <= "0010";
            when "10" => d <= "0100";
            when "11" => d <= "1000";
        end case;
    end process;
end arch;
```

Exercises Chapter 4

1. *Simulate the behavioral description of a 2 to 4 decoder in Quartus.*

I have pasted an image of the simulation at the end of this document.

2. Implement the 2 to 4 decoder on the Danjel board

I have no access to such board at the moment.

Self Test Chapter 5

1. What does a concurrent assignment mean?

Concurrent assignment means that the assignment is happening at the same time to something else.

Exercises Chapter 5

1. Simulate the 7 segments display model.

TODO

2. Design a 4-bit even parity checker (structured) and simulate it.

The source code is put below and the simulation results can be found at the end of this document.

3. Implement the parity checker and the 7 segm display on the max 10 board

I have no access to such board at the moment.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity parity_checker is
port (
    data: in std_logic_vector(3 downto 0);
    output: out std_logic
);
end parity_checker;

architecture arch of parity_checker is
    component xor_gate is
        port (
            a, b: in std_logic;
            output: out std_logic
        );
    end component;
    -- intermediate results
    signal a, b: std_logic;
begin
    u1: xor_gate port map (data(0), data(1), a);
    u2: xor_gate port map (data(2), a, b);
    u3: xor_gate port map (data(3), b, output);
end arch;
```

Simulation Results

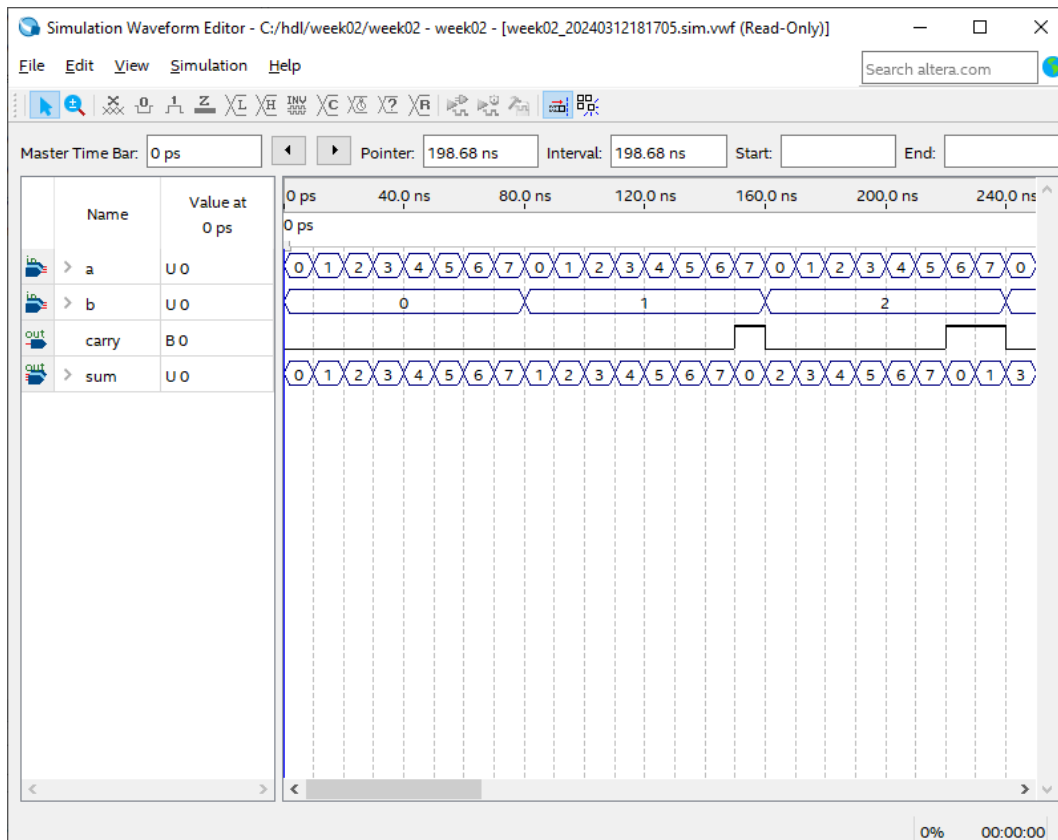


Figure 1. Simulation of Behavioral Half Adder

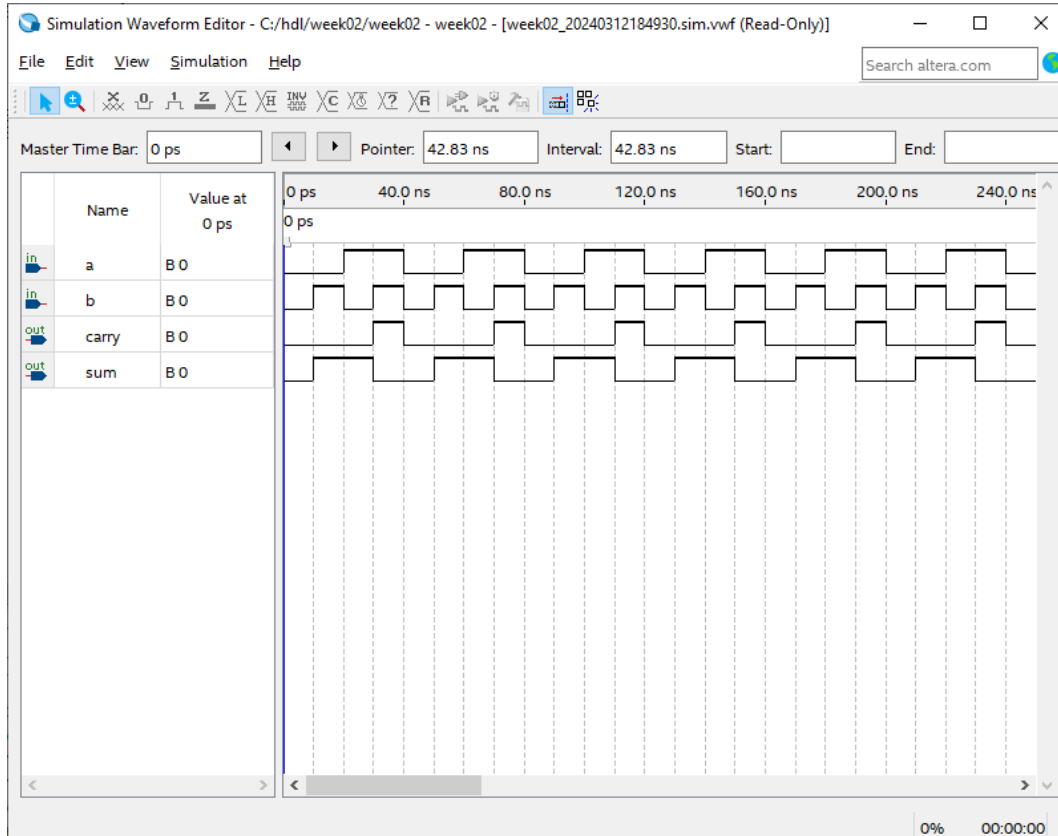


Figure 2. Simulation of Structural Half Adder

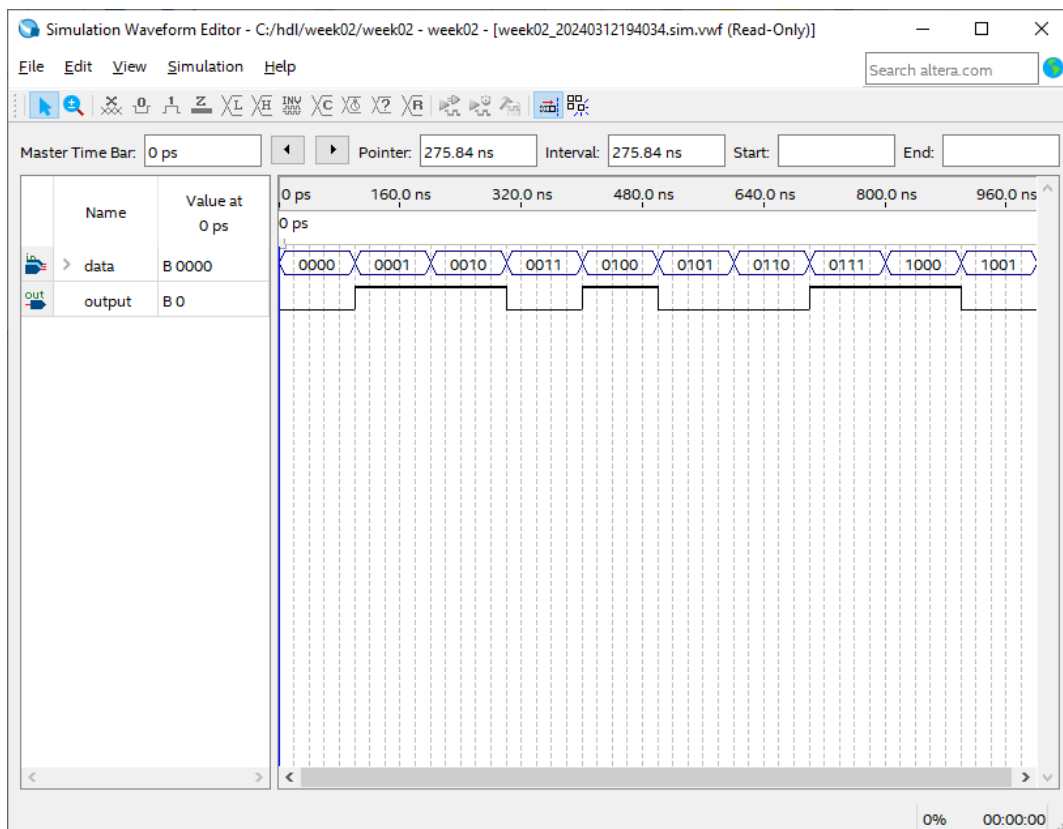


Figure 3. Simulation of Even Parity Checker